

## Chapter 4 Solutions

4.6  $I_0 = 0.3871 \text{ ma}$

4.9  $V_0 = 6.8571 \text{ Volts}$

4.14  $I_0 = -0.3 \text{ ma}$

4.19  $I_0 = 0.6667 \text{ ma}$

4.25  $V_0 = 8 \text{ Volts}$

4.29  $I = 0.3871 \text{ ma}$  ( $R_{TH} = 4.33 \text{ k}\Omega$ ,  $V_{TH} = 4 \text{ Volts}$ )

4.32  $I_0 = 1.25 \text{ ma}$  ( $R_{TH} = 2 \text{ k}\Omega$ ,  $V_{TH} = 10 \text{ Volts}$ )

4.55  $R_L = 20/9 \text{ k}\Omega$ ,  $P = 3.2 \text{ mW}$  ( $R_{TH} = \frac{20}{9} \text{ k}\Omega$ ,  $V_{TH} = \frac{32}{6} \text{ Volts}$ )

4.56  $R_L = 8 \text{ k}\Omega$ ,  $P = 2.5312 \text{ mW}$  ( $R_{TH} = 8 \text{ k}\Omega$ ,  $V_{TH} = 9 \text{ Volts}$ )

4.58  $R_L = 2 \text{ k}\Omega$ ,  $P = 12.5 \text{ mW}$  ( $R_{TH} = 2 \text{ k}\Omega$ ,  $V_{TH} = 10 \text{ Volts}$ )